

INTRODUCTION TO BASIC LOGIC GATES

Learning Objective:

Practice implementing and verifying basic logic gates.

Pre-Lab:

None

Laboratory:

Procedure you need follow to complete and verify the truth table for all the logic gates:

1. Connect the NI ELVIS board with the power supply
2. Mount the corresponding 74LS.....IC on the board.
3. Connect the IC first by connecting pin 14 to +5 V and pin 7 to GND.
4. Wire the circuit according to the diagram by consulting the corresponding gate ICs data sheet.
5. Apply all the combinations of inputs and observe the output on the LED to complete and verify the truth tables of the gates.

1. Check the operation of OR gate (IC 74LS32)


Equipment Required:

1. 74LS32

Symbolic diagram:



Pin Configuration:

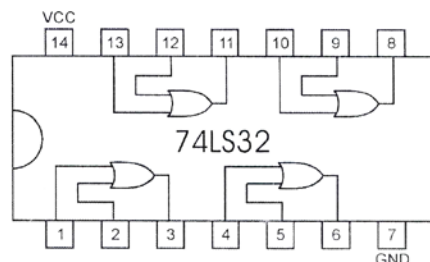

Truth Table:


Input		Output
A	B	C

Check the operation of AND gate(IC 74LS08)

Equipment Required:

2. 74LS08


Symbolic diagram:

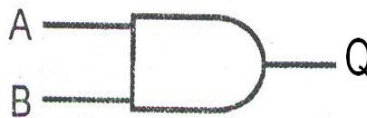

Truth Table:

Input		Output
A	B	Q

Pin Configuration:

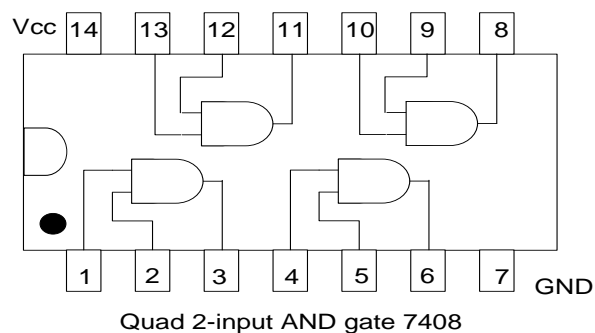


Check the operation of NOT gate (IC 74LS04)

Equipment Required:

1. 74LS04


Symbolic diagram:

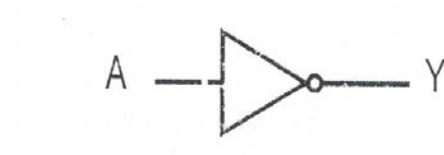

Truth Table:

Input	Output
A	Y

Pin Configuration:

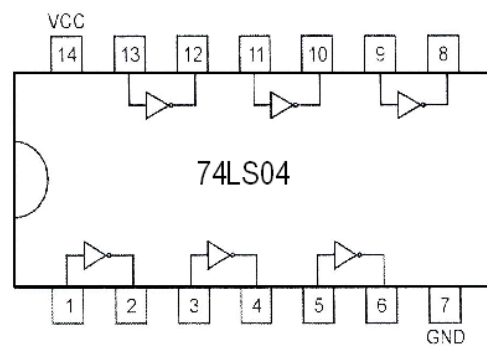

Check the operation of NOR gate (IC 74LS02)

Equipment Required:

3. 74LS02


Symbolic diagram:



Truth Table:

Input		Output
A	B	C'

Pin Configuration:

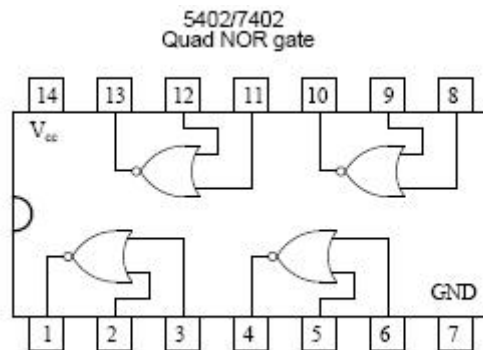

Check the operation of NAND gate(IC 74LS00).

Equipment Required:

4. 74LS00


Symbolic diagram:



Truth Table:

Input		Output
A	B	Q'

Pin Configuration:

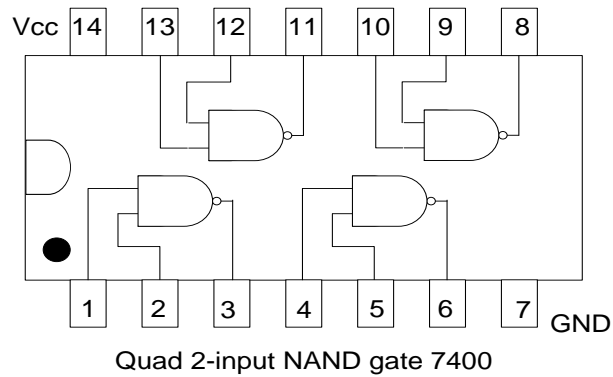

Check the operation of XOR gate (IC 74LS86)

Equipment Required:

5. 74LS86




Symbolic diagram:

Truth Table:

Input		Output
A	B	X

Pin Configuration

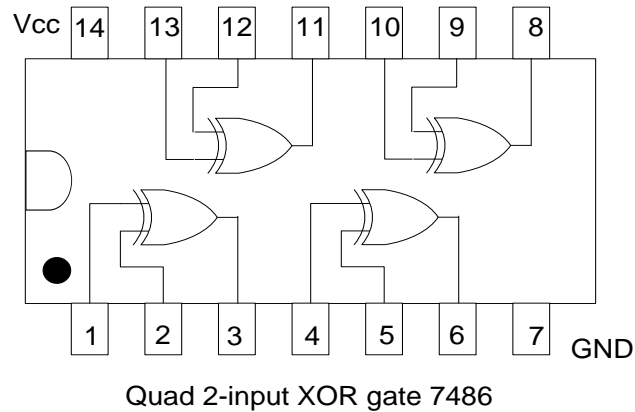

Conclusion:

Lab performed on (date): _____ Signature: _____

Checked by: _____ Date: _____

Marks Awarded: _____