

You are expected to solve homework problems individually. If needed, you may seek help from your friends. However, do not copy. Show all steps with your solutions for full credit.

Name: Key

/ 50

1) (10 points) Simplify the following Boolean functions, using three-variable maps:

a) $F(x, y, z) = \sum(2, 3, 4, 5)$

		yz			
		00	01	11	10
x	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6


$$F = xy' + x'z$$

b) $F(x, y, z) = \sum(1, 2, 3, 5, 6, 7)$


		yz			
		00	01	11	10
x	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

$$F = y + z$$


c) $F(x, y, z) = \sum(0, 2, 4, 6)$

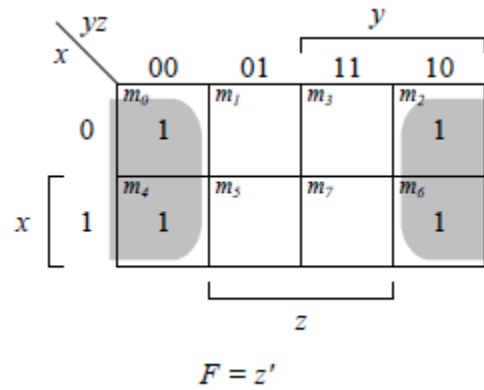

d) $F(x, y, z) = \sum(3, 4, 5, 6, 7)$

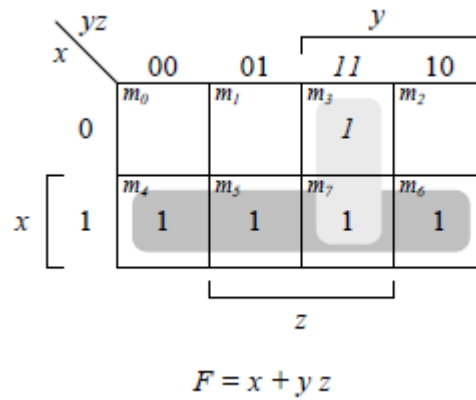


e) $F = x'y + yz' + y'z'$

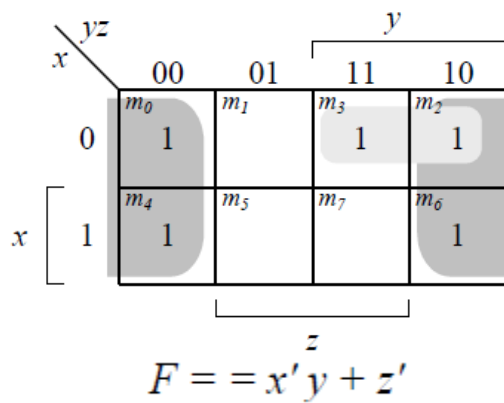


2) (16 points) Simplify the following Boolean functions, using four-variable maps:

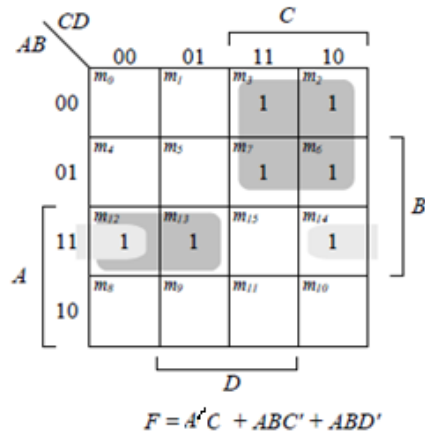
a) $F(A, B, C, D) = \sum(2, 3, 6, 7, 12, 13, 14)$



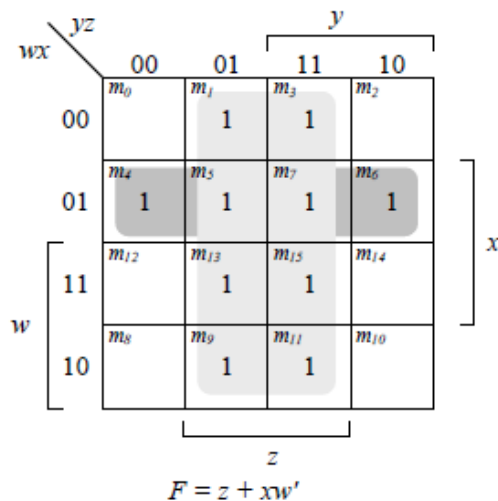
b) $F(w, x, y, z) = \sum(1, 3, 4, 5, 6, 7, 9, 11, 13, 15)$



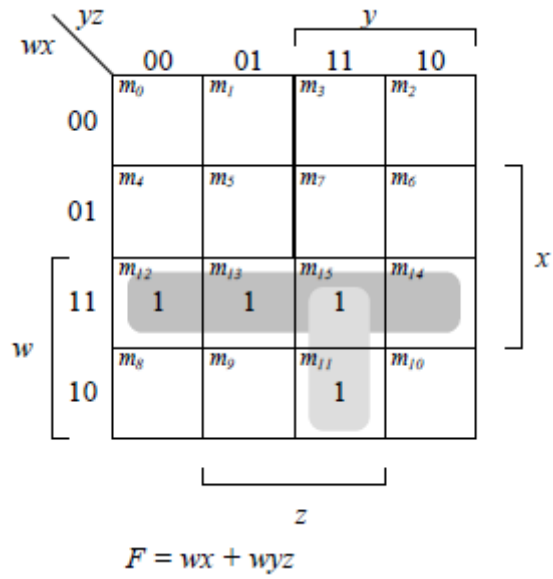c) $F(w, x, y, z) = \sum(11, 12, 13, 14, 15)$




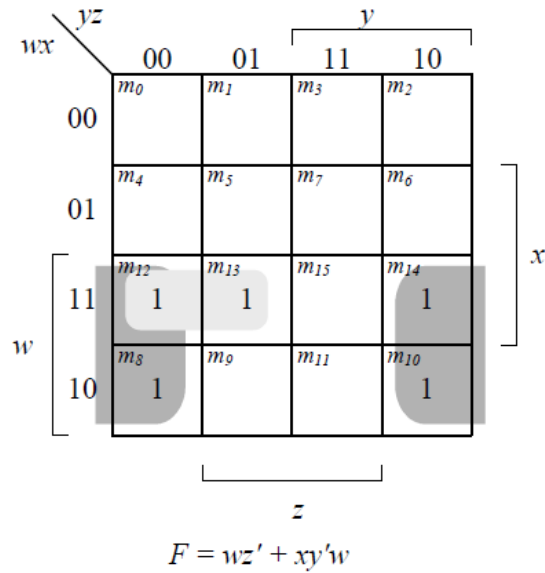d) $F(w, x, y, z) = \sum(8, 10, 12, 13, 14)$




3) (12 points) Simplify the following Boolean expressions, using four-variable maps:

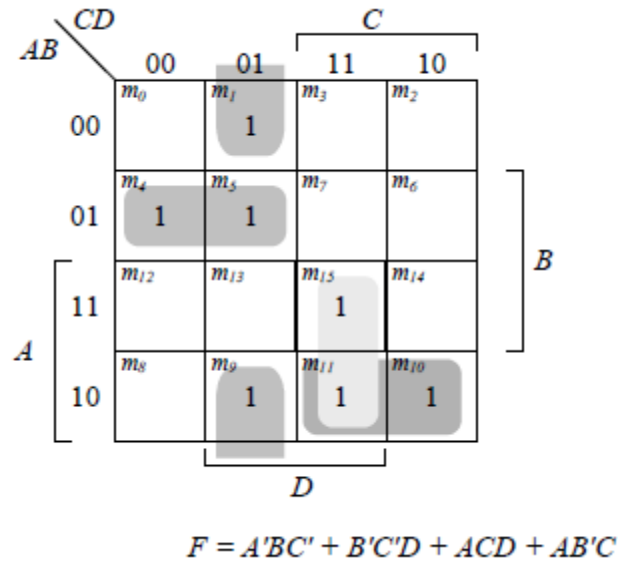
a. $A'B'C'D + AB'D + A'BC' + ABCD + AB'C$



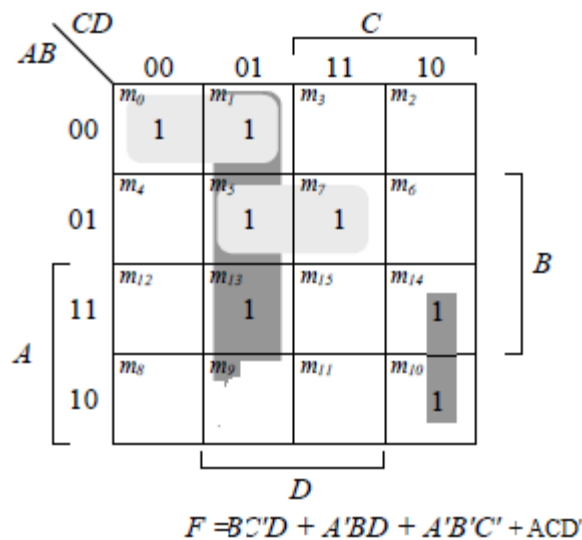
b. $A'B'C'D' + BC'D + A'C'D + A'BCD + ACD'$



c. $AD' + B'C'D + BCD' + BC'D$

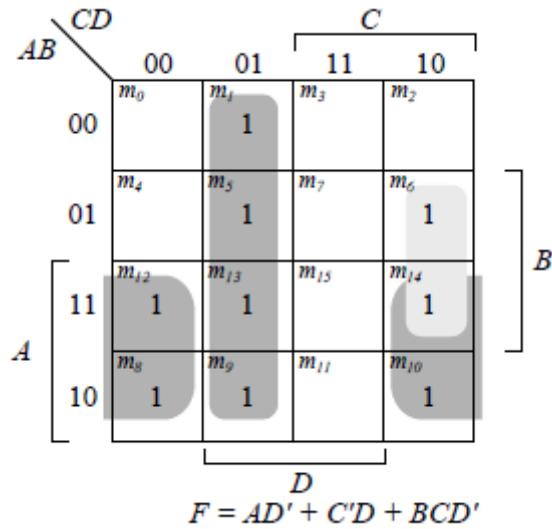

d. $wxy + xz + wx'z + w'x$

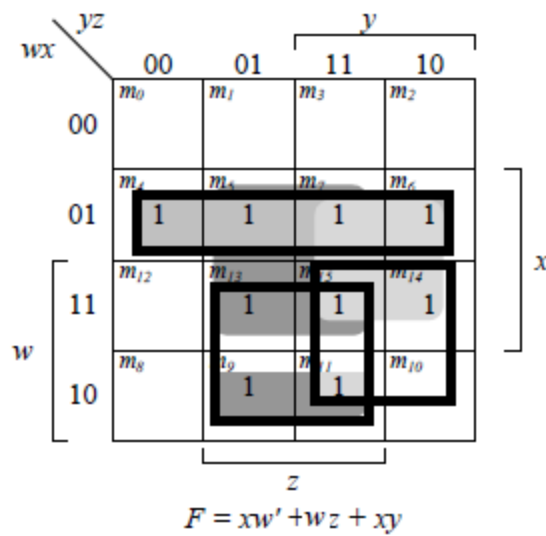

- 4) (12 points) Simplify the following Boolean function F , together with the don't-care conditions d .

a. $F(x, y, z) = \sum(0, 1, 4, 5, 6)$
 $d(x, y, z) = (2, 3, 7)$

		y			
		00	01	11	10
x	0	m_0 1	m_1 1	m_3 x	m_2 x
	1	m_4 1	m_5 1	m_7 x	m_6 1


$$F = 1$$

b. $F(A, B, C, D) = \sum(5, 6, 7, 12, 14, 15)$
 $d(A, B, C, D) = \sum(3, 9, 11)$

		C			
		00	01	11	10
AB	00	m_0	m_1	m_3 x	m_2
	01	m_4	m_5 1	m_7 1	m_6 1
A	11	m_{12} 1	m_{13}	m_{15} 1	m_{14} 1
	10	m_8	m_9 x	m_{11} x	m_{10}

$$F = BC + ABD' + A'BD$$

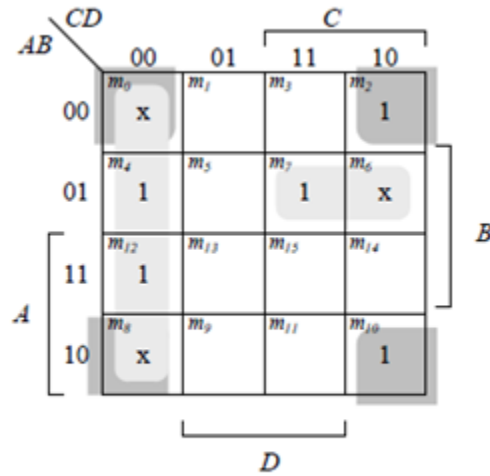- c. $F(A, B, C, D) = \sum(4, 12, 7, 2, 10)$
d. $d(A, B, C, D) = \sum(0, 6, 8)$



$$F = B'D' + C'D' + A'BC$$