

Sequential Logic


- In *Combinational Circuit*, the outputs at any instant of time are entirely dependent upon the inputs present at that time.
- A **Sequential Circuit** consists of a *Combinational Circuit* to which a **memory elements** are connected to form a feedback path.
- The **memory elements** are devices capable of storing binary information within them.
- The binary information stored in the memory elements at any given time defines the state of the sequential circuit.

In foot ball game,


- The score of the goals = the pervious goals (**state**) + new goal (**input**)
 - For example if you have pervious goal score of 5 and there's a new goal then the final score will be 6
 - Past state = 5 scores, and input = 1 score
- So, the new score state will be $= 5 + 1 = 6$ scores|

Sequential Circuit

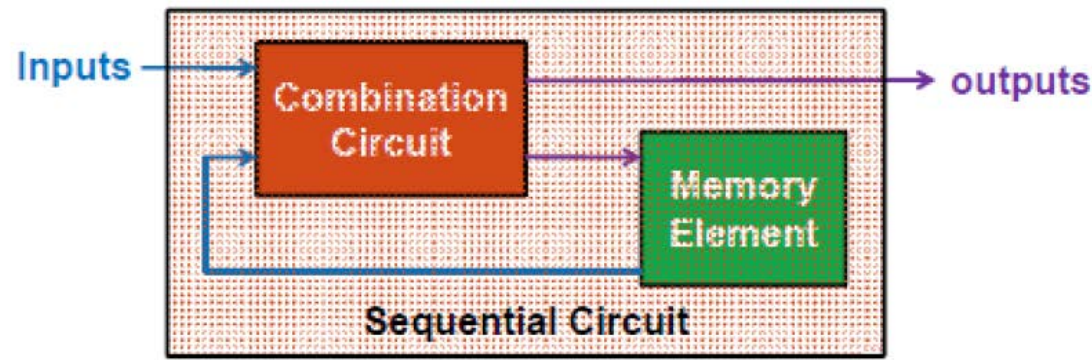- The sequential circuit receives *binary information* from *external inputs*, together with *the present state of the memory elements*, determine the binary value at *the output terminals*.
- They also determine the condition for *changing the state in the memory elements*.



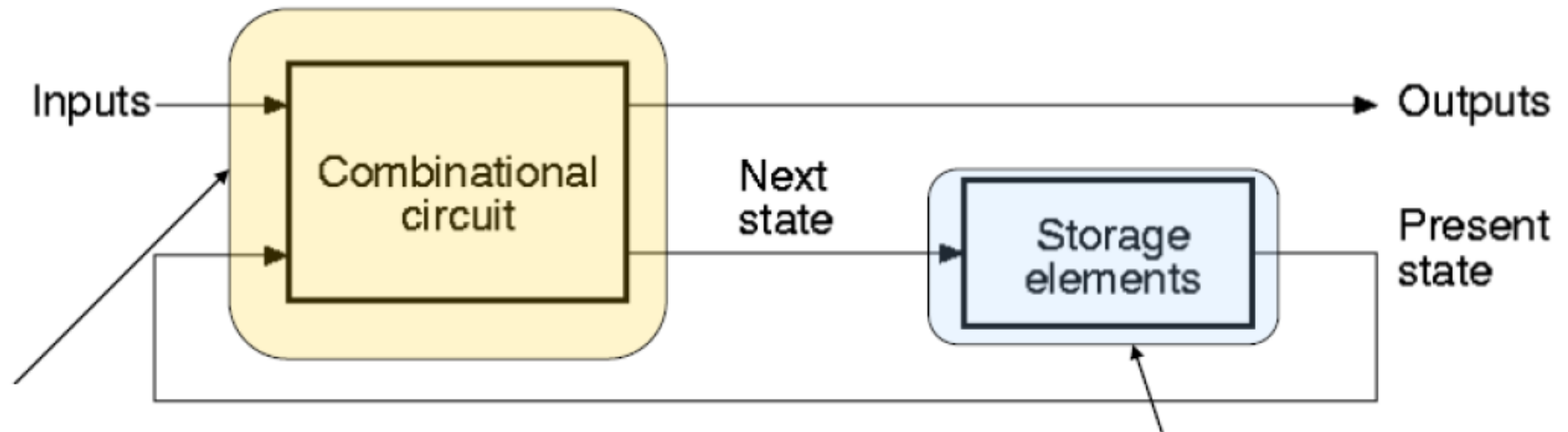- A circuit with memory, whose outputs depend on the **current input** and the **sequence of past inputs**, is called a sequential circuit.
- The behaviour of such a circuit may be described by a **state table** that specifies its **output** and **next state** as functions of its **current state** and **input**.



Sequential Circuit

- A Sequential Circuit is specified by a time sequence of inputs, outputs and internal states.
- Classification of Sequential Circuits depend on the timing of their signals.
- Types of Sequential Circuits:
 - **Synchronous:** a sequential circuit whose behavior can be defined from the knowledge of its signals at a discrete instance of time.
 - **Asynchronous:** a sequential circuit whose behavior depends on the order in which its input signals change and can be affected at any instance of time.

Storage elements

- What's required from storage element?
 - Store data (hold)
 - Accept writing a new data (write)

Types of storage (memory) elements

Memory Elements

Latch

— SR Latch

— D Latch

Flip flop

— Edge triggered (D flip-flop)

— Master-slave

— D flip-flop


— JK flip-flop

— T flip-flop

Sequential Logic : Memory Element


- The memory elements used in clocked sequential circuits are called **Flip-Flops**.
- Flip-flop circuits are binary cells capable of storing one bit of information.
- A *flip-flop* circuit has two outputs, one for normal output and one for the complement value of the bit stored in it.
- Binary information can enter a flip-flop in a variety of ways.

SR Flip Flop logic Symbol

 

- The SR Flip Flop has two inputs, SET (S) and RESET (R).
- The SR Flip Flop has two outputs, Q and \bar{Q}
- The Q output is considered the normal output and is the one most used.
- The other output \bar{Q} is simply the complement of output Q.


NAND GATE LATCH

 

SR NAND (Active LOW) Logic circuit.

- The NAND gate version has two inputs, SET (S) and RESET (R).
- Two outputs, Q as normal output and \bar{Q} as inverted output and feedback mechanism.
- The feedback mechanism is required to form a sequential circuit by connecting the **output** of **NAND-1** to the **input** of **NAND-2** and vice versa.
- The circuit outputs depends on the inputs and also on the outputs.


NOR GATE LATCH

 


SR NOR
(Active HIGH) Logic circuit

- The latch circuit can also be constructed using two NOR gates latch.
- The construction is similar to the NAND latch except that the normal output **Q** and inverted output **\bar{Q}** have reversed positions.

 - The outputs of the latch are Q and Q',
- After each write operation there must be a hold operation to store the data,
- Each cell store only one bit.



 
Write '0' into the
memory cell
(Reset State)



Hold the written
data in the memory
cell (Hold State)



2 Input NOR gate		
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0



S	R	Q	\bar{Q}	STATUS
0	0	Q	\bar{Q}	HOLD (NoChange)
0	1	0	1	RESET
1	0	1	0	SET
1	1	0	0	INVALID

Clocked RS Flip-Flop

  - The graphic symbol for Clocked RS flip-flop is



- The Clock Pulse is marked with small triangle.
- The triangle is a symbol for ***dynamic indicator*** and denotes the fact that the flip-flop responds to an input clock transition from a low-level (binary 0) to a high-level (binary 1)

SR flip flop

Truth table

clk	S	R	Q_{n+1}
0	X	X	Q_n
1	0	0	Q_n
1	0	1	0
1	1	0	1
1	1	1	Invalid

Characteristic Table



Q_n	S	R	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X

Excitation Table:

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

D Flip Flop

  A D flip-flop is a modification of the Clocked RS flip-flop.



D flip-flop

Truth table:

clk	D	Q_{n+1}
0	X	Q_n
1	0	0
1	1	1

Characteristic table:


Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

Excitation Table


Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

Positive and Negative Edge D Flip-Flop

 - D flops can be triggered on positive or negative edge
- Bubble before **Clock (C)** input indicates **negative edge trigger**




(a) Positive-edge

 

(a) Negative-edge


Fig. 5-11 Graphic Symbol for Edge-Triggered *D* Flip-Flop

 

Lo-Hi edge




Hi-Lo edge

 

D	CLK	Q
0	↑	0
1	↑	1


(a)

 


(b)

JK Flip Flop

JK Flip-Flop

 

Graphic Symbol

 

JK flip flop

Truth table:

clk	J	K	Q_{n+1}
0	x	x	Q_n
1	0	0	Q_n
1	0	1	0
1	1	0	1
1	1	1	\bar{Q}_n (toggle)


} Memory

Excitation table:

Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Characteristic Table


Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	$\overline{Q_0}$ (toggles)


(a)

Characteristic Table

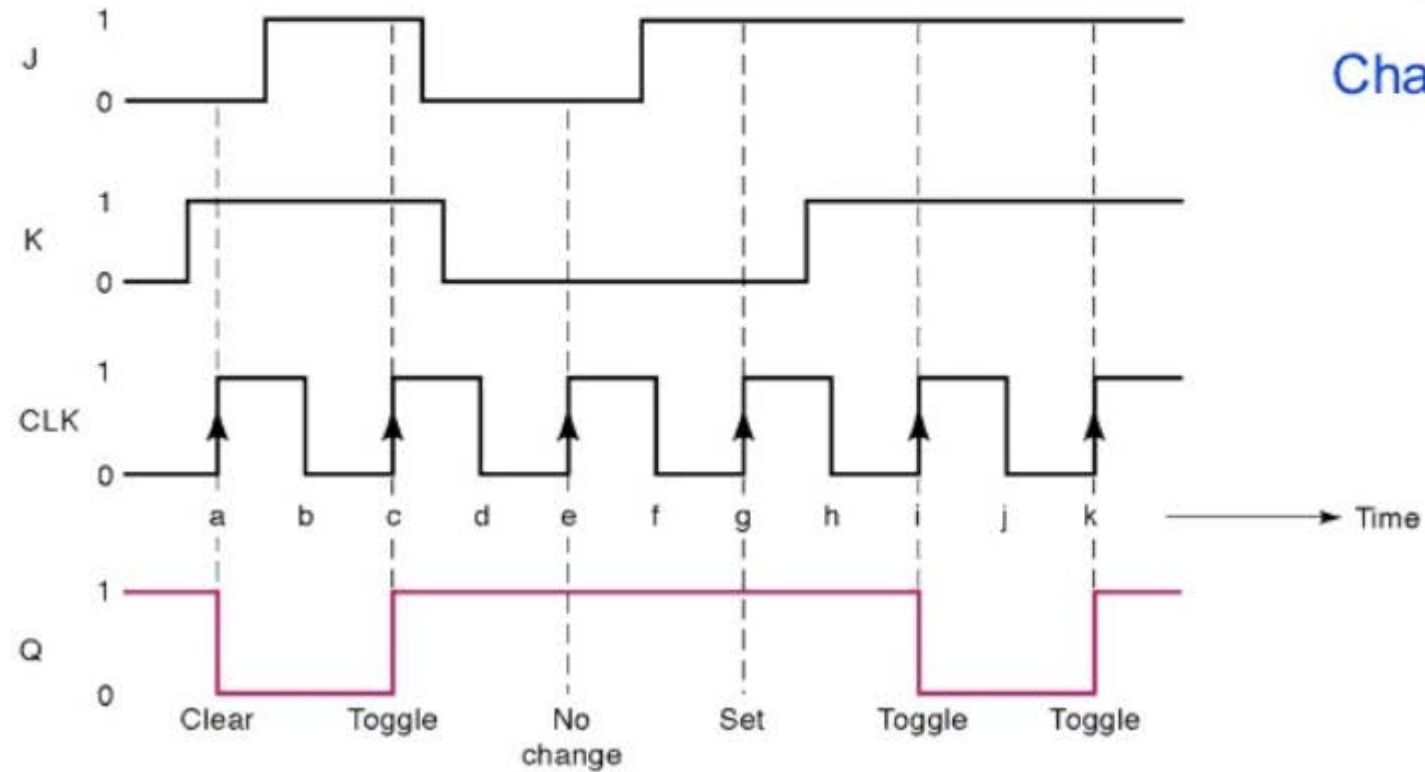

Asynchronous Inputs


 
- J, K are synchronous inputs
 - Effects on the output are synchronized with the *CLK* input.
- Asynchronous inputs operate independently of the synchronous inputs and clock
 - Set the FF to 1/0 states *at any time*.



PRESET	CLEAR	FF response
1	1	Clocked operation*
0	1	Q = 1 (regardless of CLK)
1	0	Q = 0 (regardless of CLK)
0	0	Not used

*Q will respond to J, K, and CLK

Asynchronous Inputs

  

(a)

Point	Operation
a	Synchronous toggle on NGT of CLK
b	Asynchronous set on $\overline{\text{PRE}} = 0$
c	Synchronous toggle
d	Synchronous toggle
e	Asynchronous clear on $\overline{\text{CLR}} = 0$
f	$\overline{\text{CLR}}$ over-rides the NGT of CLK
g	Synchronous toggle

T flip flop

Truth table:

clk	T	Q_{n+1}
0	X	Q_n (memory)
1	0	Q_n
1	1	\bar{Q}_n (toggle)

Characteristic table

Q_n	T	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0


Excitation Table:

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0




Master Slave Flip Flop

 schematic diagram of master slave J-K flip flop




Master Slave JK Flip Flop

Master slave using SR Latch

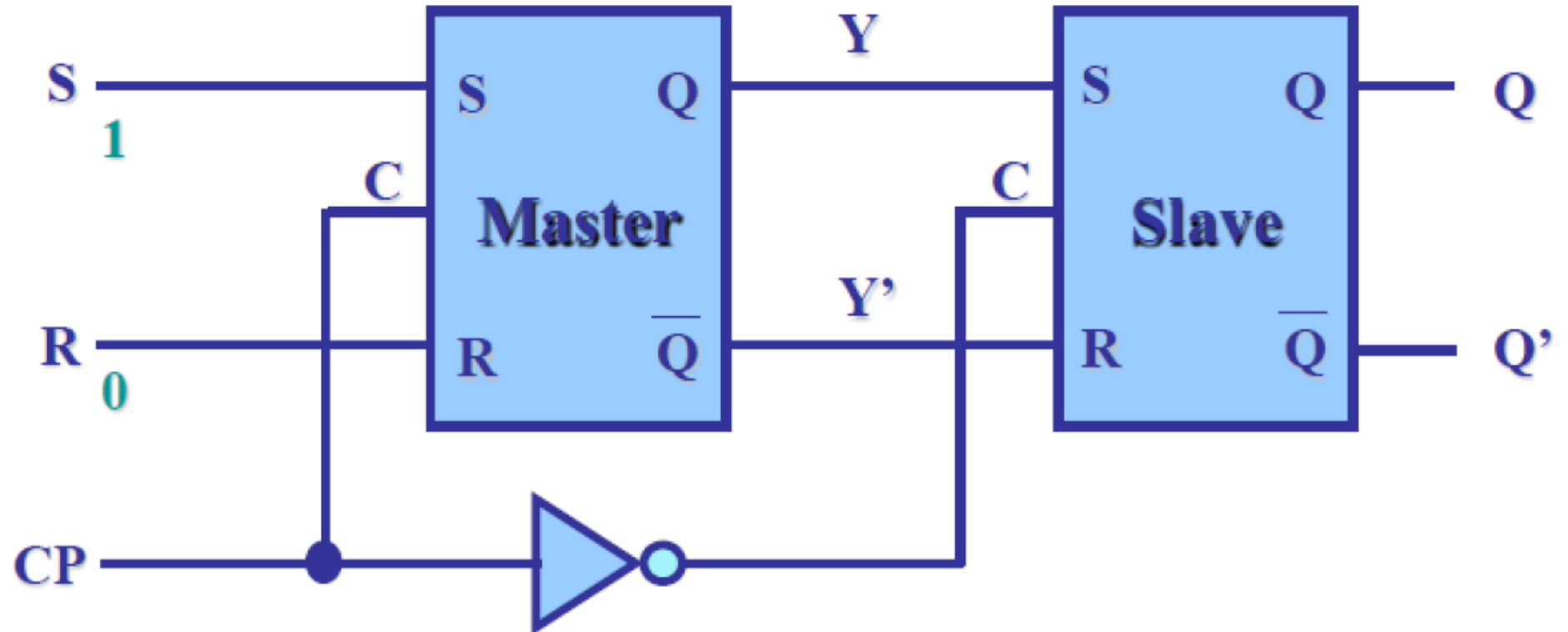

Master-Slave using D Flip-Flop

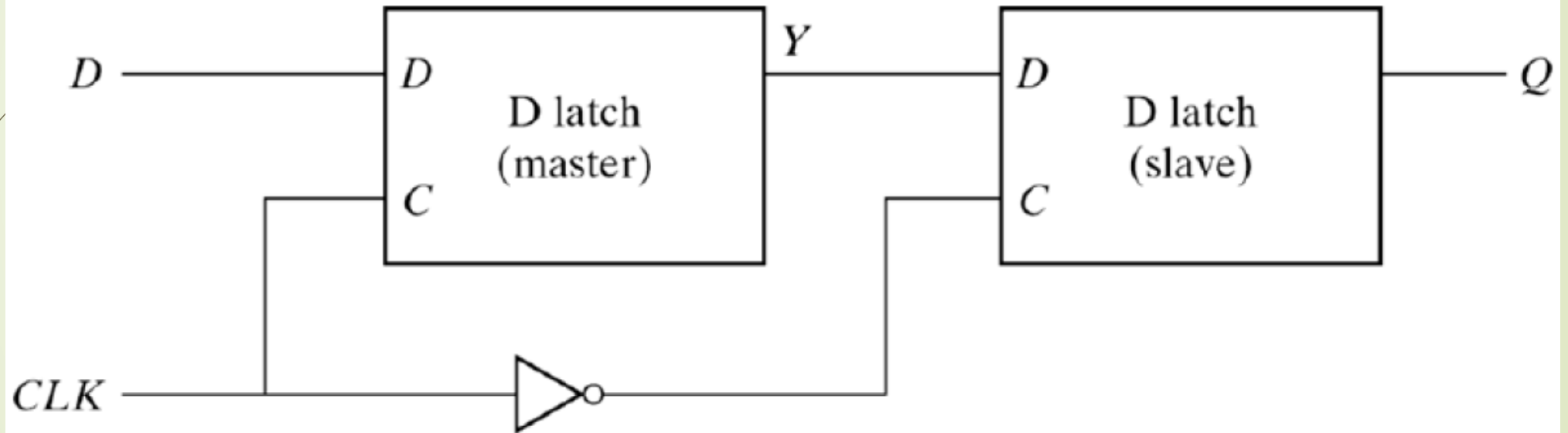



Thanks to Ali Mustafa for the slides