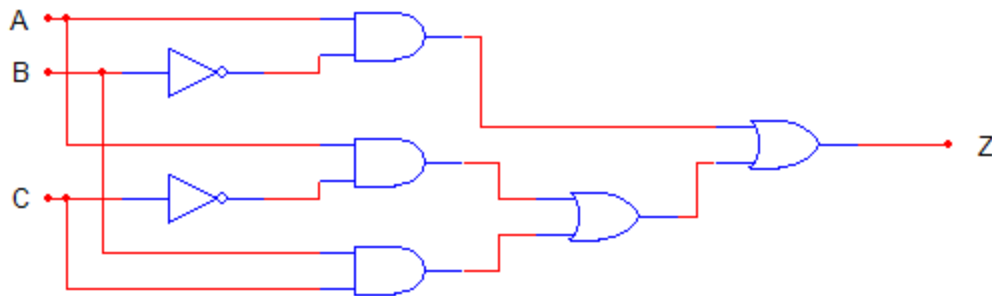


Circuit Simplification: Boolean Algebra

What is Boolean Algebra ?


Boolean Algebra is a mathematical technique that provides the ability to algebraically simplify logic expressions. These simplified expressions will result in a logic circuit that is equivalent to the original circuit, yet requires fewer gates.



$Z = BC + A\bar{B} + A\bar{C}$


**Simplification
With Boolean
Algebra**

$Z = A + BC$

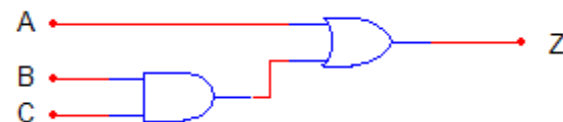

George Boole

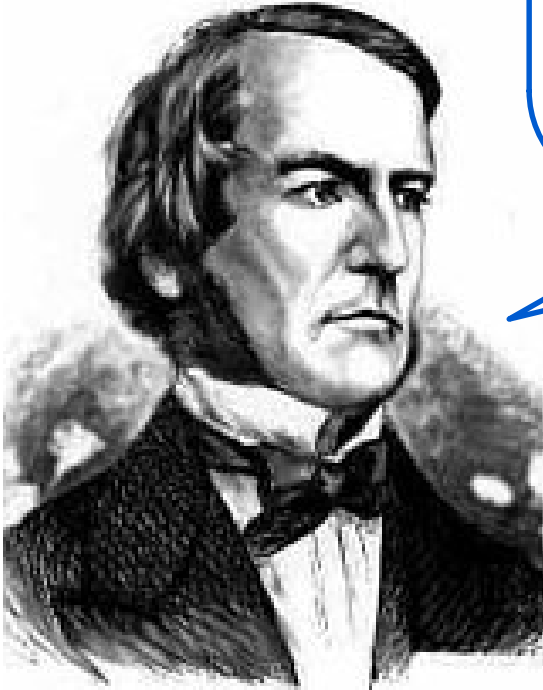My name is George Boole and I lived in England in the 19th century. My work on mathematical logic, algebra, and the binary number system has had a unique influence upon the development of computers. Boolean Algebra is named after me.




Boolean Theorems

Single Variable - Invert Function

Theorem #9

$$\overline{\overline{X}} = X$$

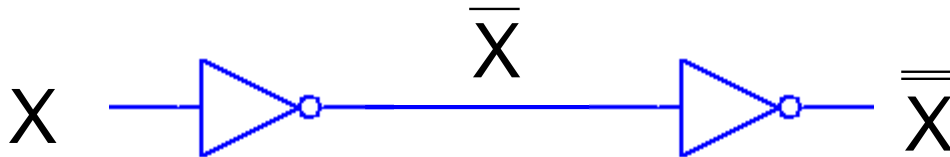

X	\overline{X}	$\overline{\overline{X}}$
0	1	0
1	0	1

Boolean Theorems

Commutative Law

Theorem #11 – AND Function

$$X \cdot Y = Y \cdot X$$

Theorem #12 – OR Function

$$X + Y = Y + X$$

Boolean Theorems

Associative Law

Theorem #13– AND Function

$$X (Y Z) = (X Y) Z$$

Theorem #14 – OR Function

$$X + (Y + Z) = (X + Y) + Z$$

Boolean Theorems

Distributive Law

Theorem #15 – AND Function

$$X (Y + Z) = X Y + X Z$$

Theorem #16 – OR Function

$$(X + Y)(W + Z) = XW + XZ + YW + YZ$$

Boolean Theorems

Consensus Theorem

Theorem #16

$$X + \overline{X}Y = X + Y$$

Summary

Boolean Theorems

1) $X \cdot 0 = 0$

2) $X \cdot 1 = X$

3) $X \cdot X = X$

4) $X \cdot \bar{X} = 0$

5) $X + 0 = X$

6) $X + 1 = 1$

7) $X + X = X$

8) $X + \bar{X} = 1$

9) $\bar{\bar{X}} = X$

10) $X \cdot Y = Y \cdot X$

11) $X + Y = Y + X$

12) $X(YZ) = (XY)Z$

13) $X + (Y + Z) = (X + Y) + Z$

14) $X(Y + Z) = XY + XZ$

15) $(X + Y)(W + Z) = XW + XZ + YW + YZ$

16) $X + \bar{X}Y = X + Y$

Commutative
Law

Associative
Law

Distributive
Law

Consensus
Theorem

Duality Principle

- A Boolean equation remains valid if we take the dual of the expressions on both sides of the equals sign
- Dual of expression it means,
 - Interchange 1's with 0's (and Vice-versa)
 - Interchange AND (.) with OR (+) (and Vice-versa)

$$X+0=X \xrightarrow{\text{Duality}} X \cdot 1=X$$

$$X+X \cdot Y=X \xrightarrow{\text{Duality}} X \cdot (X+Y)=X$$

$$X+X=X \xrightarrow{\text{Duality}} X \cdot X=X$$

$$X+X \cdot Y=X \xrightarrow{\text{Duality}} X \cdot (X+Y)=X$$

Find the complement of the functions

$$F_1 = x'yz' + x'y'z.$$

$$F_2 = x(y'z' + yz).$$

1. $F_1 = x'yz' + x'y'z.$

The dual of F_1 is $(x' + y + z')(x' + y' + z).$

Complement each literal: $(x + y' + z)(x + y + z') = F_1'.$

2. $F_2 = x(y'z' + yz).$

The dual of F_2 is $x + (y' + z')(y + z).$


Complement each literal: $x' + (y + z)(y' + z') = F_2'.$

DeMorgan's Law


Theorem 1: NAND = Bubbled OR

Complement of product is equal to addition of the compliments.
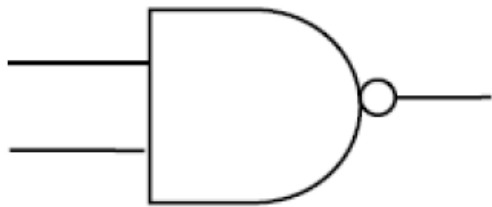
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$




\equiv

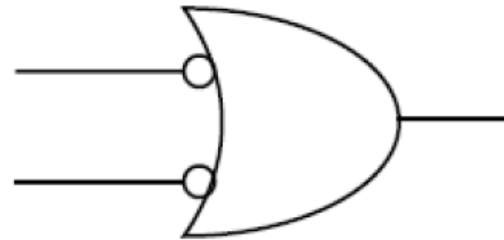


Theorem 2: NOR = Bubbled AND

is equal to product of the compliments.
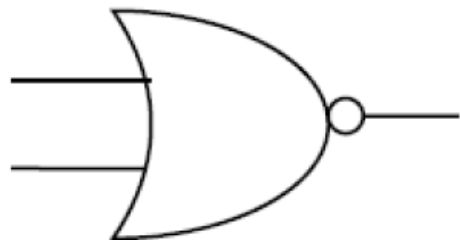
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



\equiv

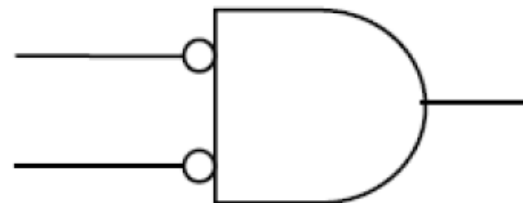

Simplify the following Boolean functions to a minimum number of literals.

1. $x(x' + y) = xx' + xy = 0 + xy = xy.$

2. $x + x'y = (x + x')(x + y) = 1(x + y) = x + y.$

3. $(x + y)(x + y') = x + xy + xy' + yy' = x(1 + y + y') = x.$

4.
$$\begin{aligned} xy + x'z + yz &= xy + x'z + yz(x + x') \\ &= xy + x'z + xyz + x'yz \\ &= xy(1 + z) + x'z(1 + y) \\ &= xy + x'z. \end{aligned}$$


Sum-of-products

- ANDed product–input combination for which output is true
- Each variable appears exactly once, in true or inverted form (but not both)

From the pervious example:

A	B	C	minterms
0	0	0	0 $A'B'C'$ m0
0	0	1	1 $A'B'C$ m1
0	1	0	0 $A'BC'$ m2
0	1	1	1 $A'BC$ m3
1	0	0	0 $AB'C'$ m4
1	0	1	1 $AB'C$ m5
1	1	0	1 ABC' m6
1	1	1	1 ABC m7

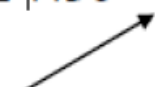short-hand notation for
minterms of 3 variables



F in canonical form:

$$\begin{aligned}
 F(A, B, C) &= \Sigma m(1,3,5,6,7) \\
 &= m1 + m3 + m5 + m6 + m7 \\
 &= A'B'C + A'BC + AB'C + ABC' + ABC
 \end{aligned}$$

canonical form \neq minimal form

$$\begin{aligned}
 F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\
 &= (A'B' + A'B + AB' + AB)C + ABC' \\
 &= ((A' + A)(B' + B))C + ABC' \\
 &= C + ABC' \\
 &= ABC' + C \\
 &= AB + C
 \end{aligned}$$

Product-of-sums

- Sum term (or maxterm)
- ORed sum of literals –input combination for which output is false
- Each variable appears exactly once, in true or inverted form (but not both)

A	B	C	maxterms	
0	0	0	$A+B+C$	M0
0	0	1	$A+B+C'$	M1
0	1	0	$A+B'+C$	M2
0	1	1	$A+B'+C'$	M3
1	0	0	$A'+B+C$	M4
1	0	1	$A'+B+C'$	M5
1	1	0	$A'+B'+C$	M6
1	1	1	$A'+B'+C'$	M7

F in canonical form:

$$\begin{aligned}
 F(A, B, C) &= \Pi M(0, 2, 4) \\
 &= M0 \cdot M2 \cdot M4 \\
 &= (A + B + C)(A + B' + C)(A' + B + C)
 \end{aligned}$$

canonical form \neq minimal form

$$\begin{aligned}
 F(A, B, C) &= (A + B + C)(A + B' + C)(A' + B + C) \\
 &= (A + B + C)(A + B' + C) \\
 &\quad (A + B + C)(A' + B + C) \\
 &= (A + C)(B + C)
 \end{aligned}$$

short-hand notation for
Maxterms of 3 variables

SOP and POS Represent the same function

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F = \sum m(1, 3, 5, 6, 7) \quad \longrightarrow \quad F = \prod M(0, 2, 4)$$

Conversion Procedure for Standard SOP

Example: Convert the expression into the standard SOP form

$$Y = AB + AC' + BC$$

Solution: Given expression $Y = AB + AC' + BC$

Step 1: Find the missing literals

$$Y = AB + AC' + BC$$

Step 2: AND each term with (Missing literal + its compliment)

$$Y = AB(C + C') + AC'(B + B') + BC(A + A')$$

Simplify the expression to get the standard SOP form

$$Y = ABC + ABC' + ABC' + AB'C' + ABC + A'BC$$



$$A + A = A$$

$$Y = ABC + ABC' + AB'C' + A'BC$$

(Each term consists of all literal)

Conversion Procedure for Standard POS


- **Example:** Convert the expression into the standard SOP form

$$Y = (A+B)(A+C)(B+C')$$

Step 1: Find the missing literals

Step 2: OR each term with (Missing literal + its complement)

$$Y = (A + B + CC')(A + BB' + C)(AA' + B + C')$$

$$Y = (A + B + C)(A + B + C')(A + B + C)(A + B' + C)(A + B + C')(A' + B + C')$$


$$Y = (A + B + C)(A + B + C')(A + B' + C)(A' + B + C')$$