 


Universal Gates and K-Mapping: Fireplace Control Circuit

The Acme Fireplace Company has hired you to redesign the fireplace control circuit for their latest residential gas fireplace. The fireplace burner is equipped with four thermal sensors that output a logic (1) whenever a flame is present. These sensors are connected to the fireplace control circuit which outputs a (1) to the emergency cut-off valve to keep the gas flowing (i.e., a zero will turn the gas off).

The original design of the fireplace control circuit was quite simple. For the gas valve to remain on, all four sensors needed to output a logic (1). During field testing it was discovered that variations in gas pressure and humidity cause the thermal sensors to occasionally output a logic (0) even when a flame was present. This caused frequent unnecessary shut downs and constant customer dissatisfaction.



For the redesign, it has been determined that the emergency cut-off valve should remain open as long as three of the four sensors indicate that a flame is present. Additionally, the designers have asked you to add a second output indicator to the control circuit. This indicator will output a logic (1) when the four sensors do not all agree (i.e., not all on or not all off). This indicator will be used by the service technician to diagnose whether a faulty sensor exists.

Procedure

Design

Design a combinational logic circuit that meets the above detailed design specifications.

Additionally:

- The Karnaugh mapping technique must be used to obtain the simplified logic expression for both outputs.

- The circuit that controls the emergency cut-off valve must be implemented using only NAND gates.
- The circuit for the possible faulty sensor indicator must be implemented using only NOR gates.

Evaluation

Test your *Fireplace Control Circuit* design in the NI ELVIS board. Use switches for the inputs **A**, **B**, **C**, and **D** and a probe or LED circuit for the two outputs. Verify that the circuit is working as designed. If it is not, review your design work and circuit implementation to identify your mistake.

Lab performed on (date): _____ Signature: _____

Checked by: _____ Date: _____

Marks Awarded: _____