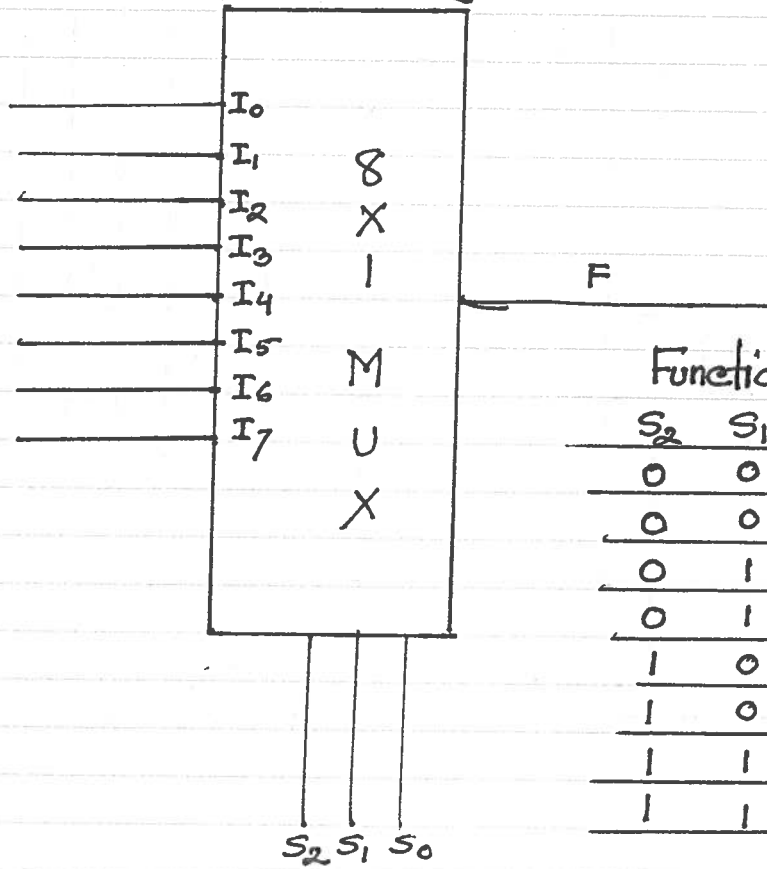


1.

# Block diagram




## Function table

$S_2$	$S_1$	$S_0$	F
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$
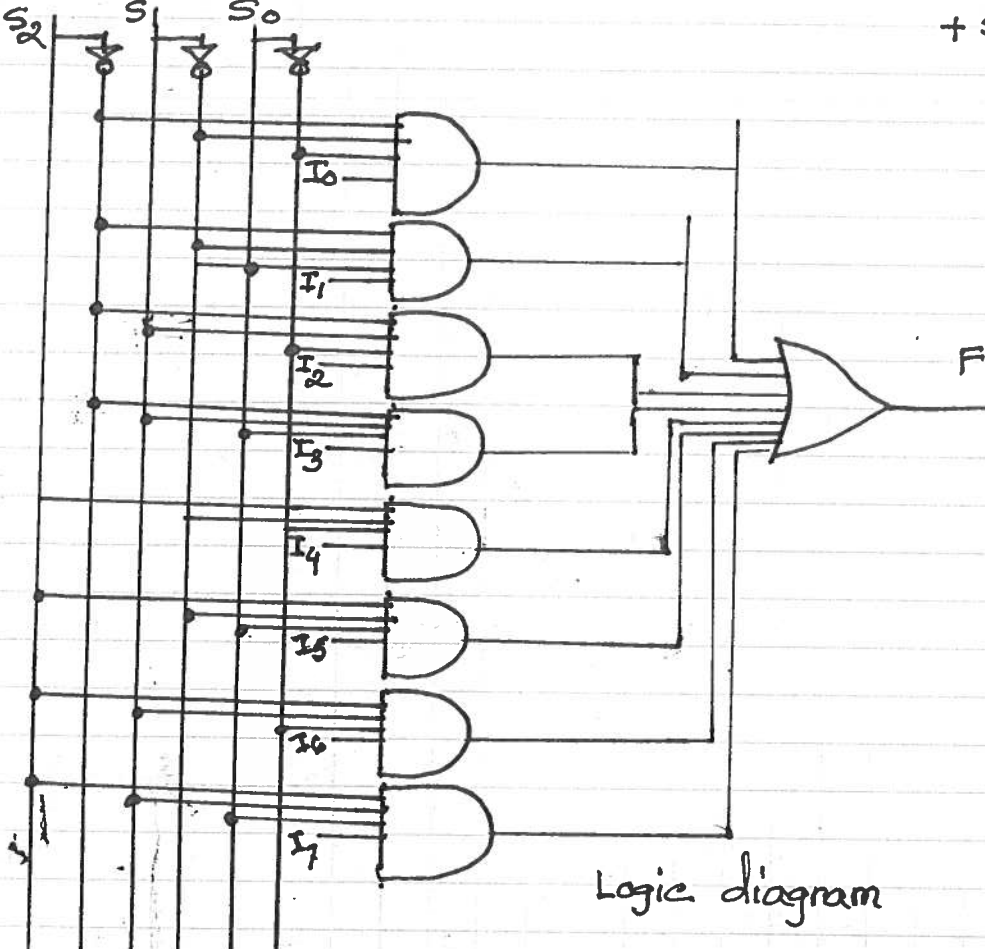
## Boolean expressions:

$$F = S_2' S_1' S_0' I_0 + S_2' S_1' S_0 I_1 + S_2' S_1 S_0' I_2 + S_2' S_1 S_0 I_3 + S_2 S_1' S_0' I_4 + S_2 S_1' S_0 I_5 + S_2 S_1 S_0' I_6 + S_2 S_1 S_0 I_7$$



## Logic diagram

## Cascading of Multiplexer:

Implementing 4x1 Mux with 2x1 Mux:

First we will determine the no. of 2x1 Mux and levels of Mux.

— We will divide the no. of inputs of the available mux by the no. of inputs of the required mux.


— In this implementation,

the no. of inputs of the required mux = 4

the no. of inputs of the available mux = 2

$$\left. \begin{array}{l} 4/2 = 2 \\ 2/2 = 1 \end{array} \right\} 2+1=3$$

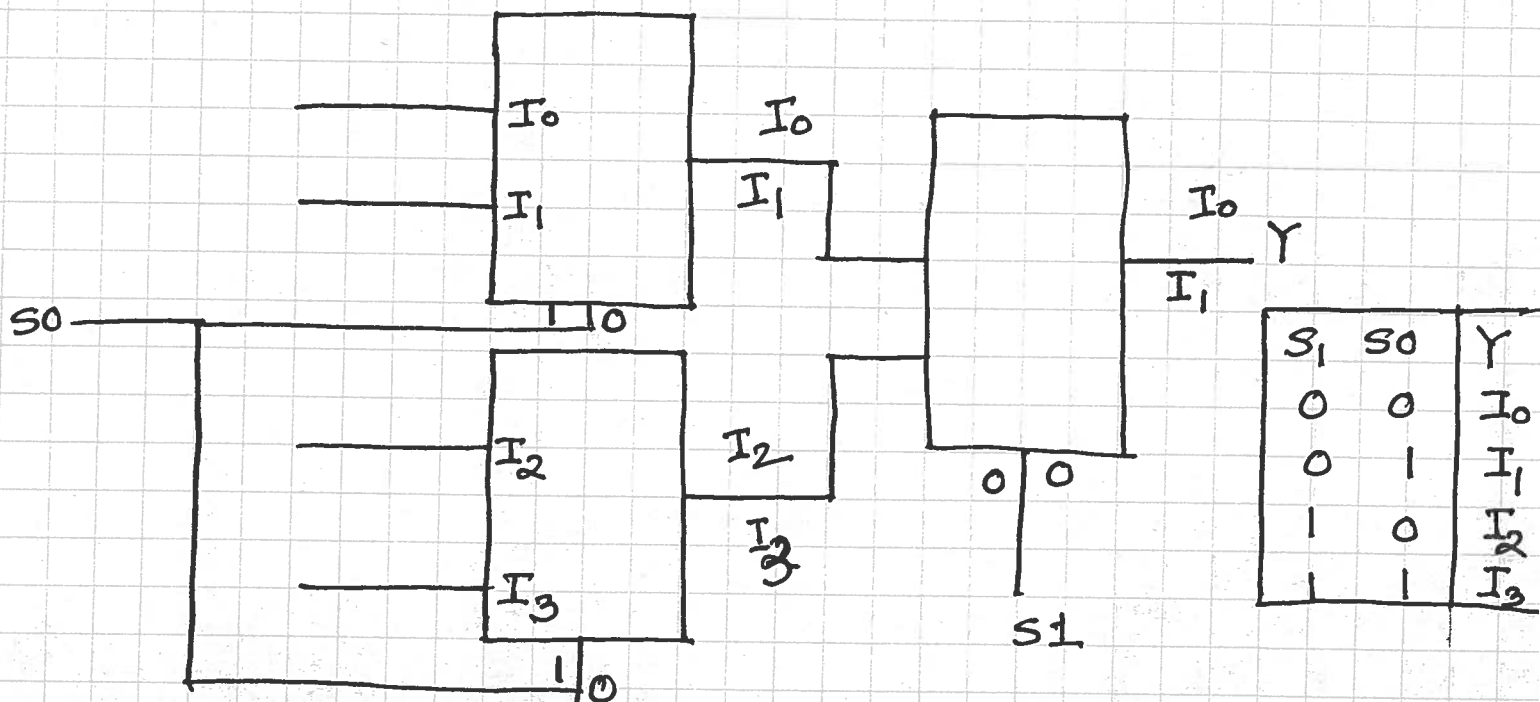So, we need 3, 2x1 Mux to implement 4x1 Mux. We also see that in the 1st level we need 2 and in the second level we need 1, 2x1 Mux.



Implementing 8X1 MUX with 2X1 Mux:

No. of inputs of the required Mux = 8


No. of inputs of the available Mux = 8

$$\frac{8}{2} = 4$$

$$\frac{4}{2} = 2$$

$$\frac{2}{2} = 1$$

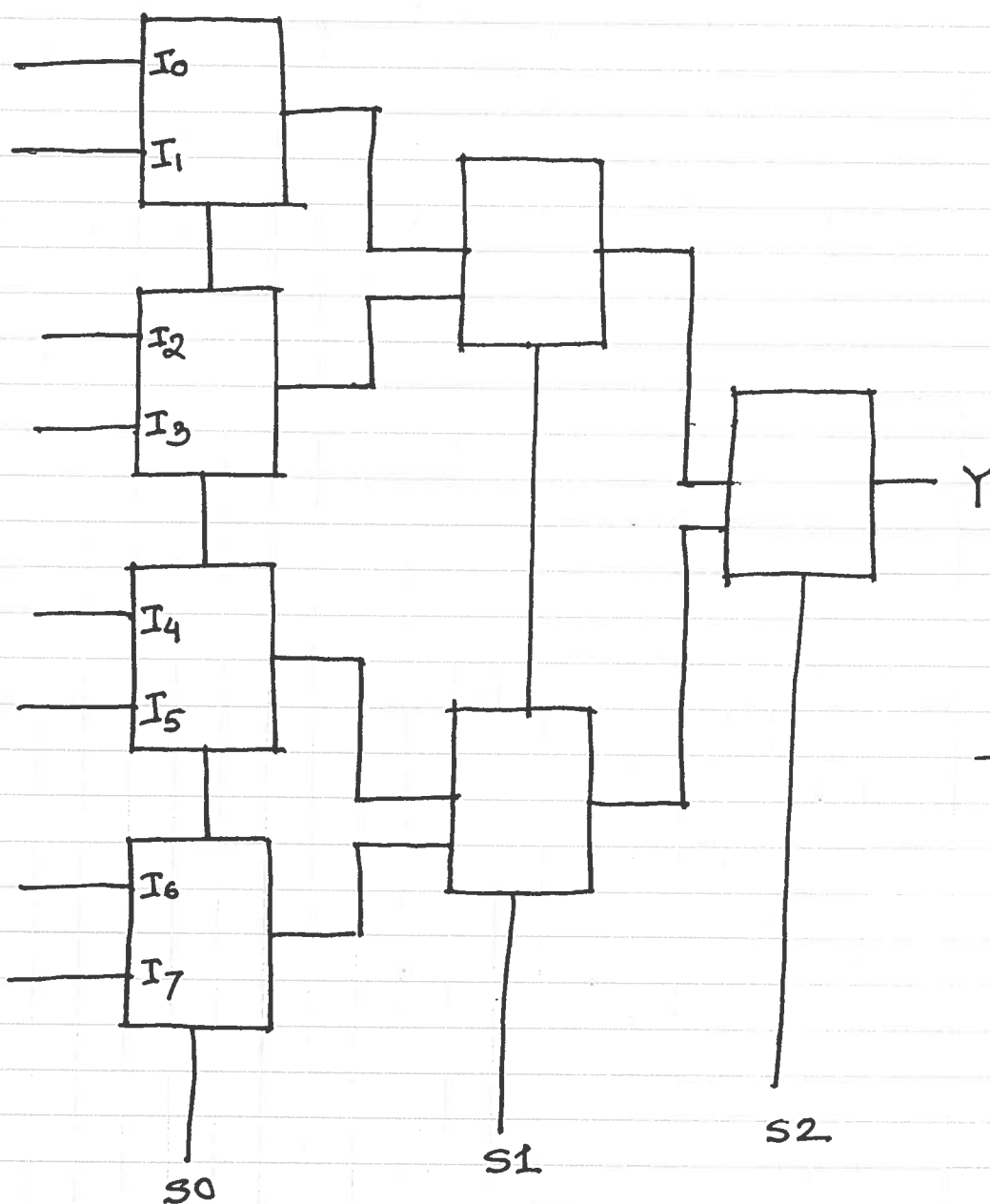
}  $4 + 2 + 1 = \text{total } 7, 2 \times 1 \text{ Mux}$   
in 3 levels.



$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$
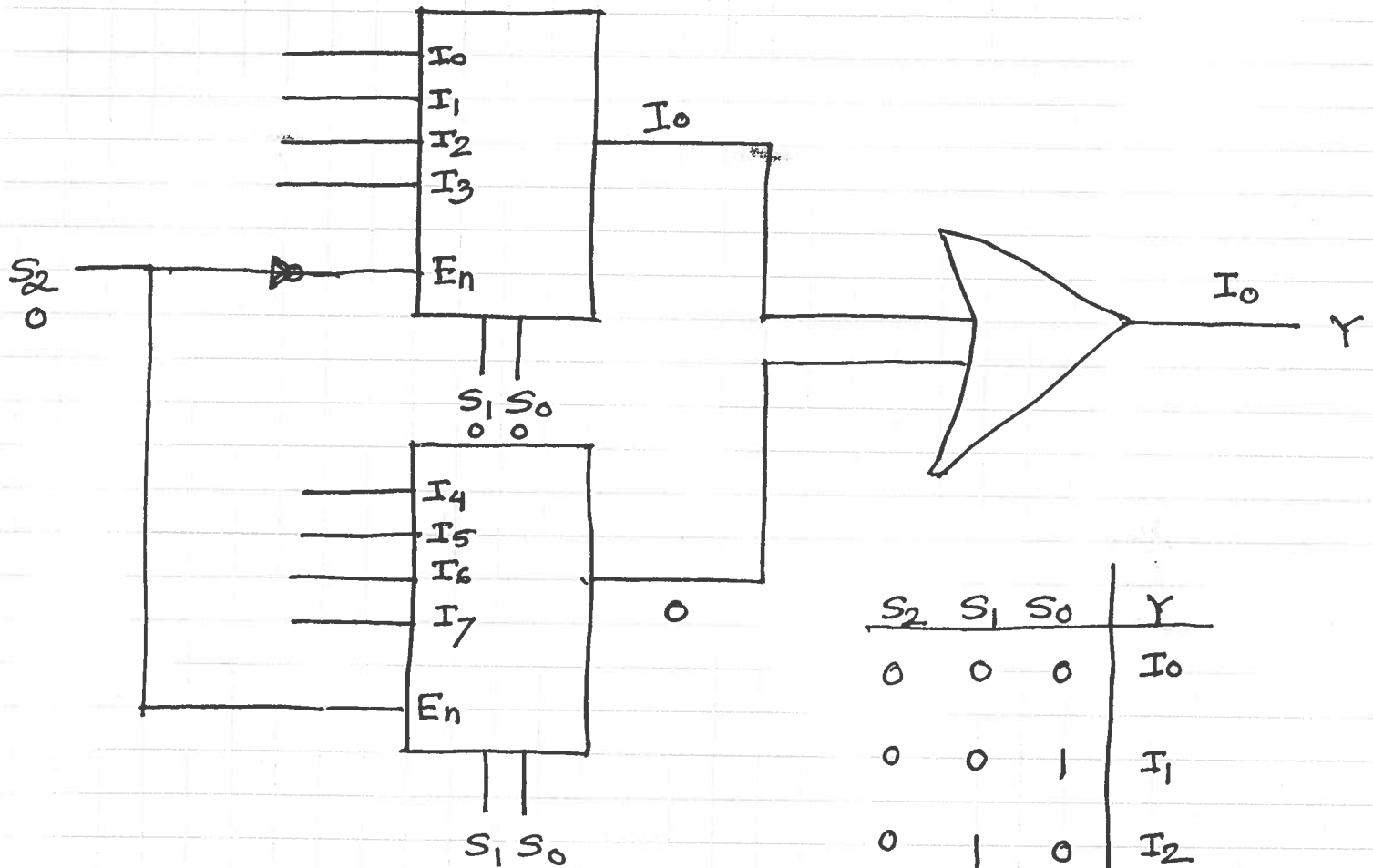
# Implementing 8X1 Mux with 4x1 Mux (Exception):

$$\left. \begin{array}{l} \frac{8}{4} = 2 \\ \frac{2}{4} = 0.5 \end{array} \right\} \text{ does not work.}$$



$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

$$F(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 13, 14)$$

Implement the function with

a) 4X1 Mux

b) 8X1 Mux

c) 16X1 Mux

a) 4X1 Mux

CD \ AB	00	01	11	10	
00	0	1	3	2	$= D' + C$
01	4	5	7	6	$= CD'$
11	12	13	15	14	$= CD + CD' = C \oplus D$
10	8	9	11	10	$= C'$

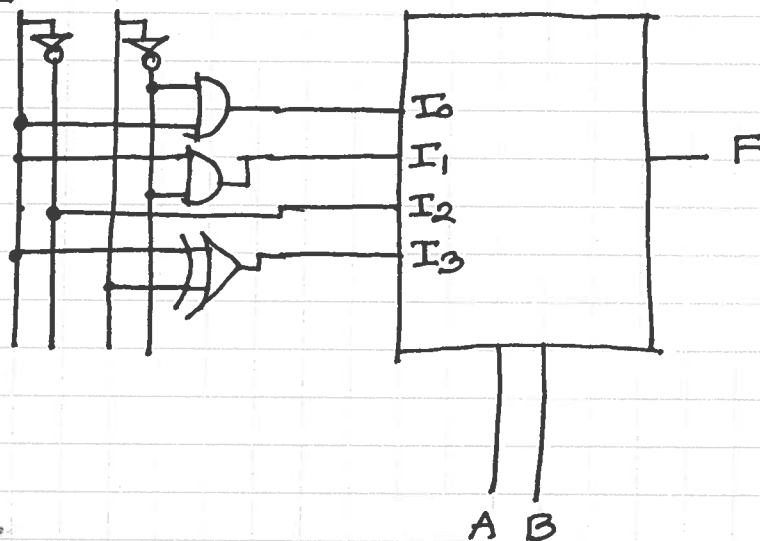


Fig: 4X1 Mux implementation using AB as select line

a)

AB \ CD	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$F(A,B,C,D) = \sum m(0,2,3,6,8,9,13,14)$$

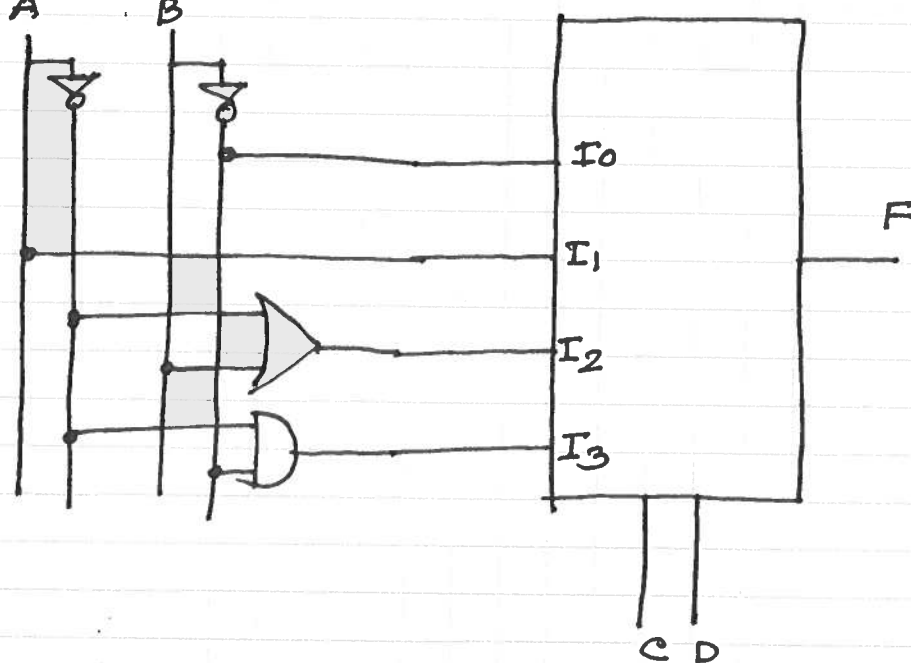


Fig. 4x1 Mux Implementation  
using CD as select line

b) 8X1 Mux

$$F(A, B, C, D) = \sum m(0, 2, 3, 4, 8, 9, 13, 14)$$

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

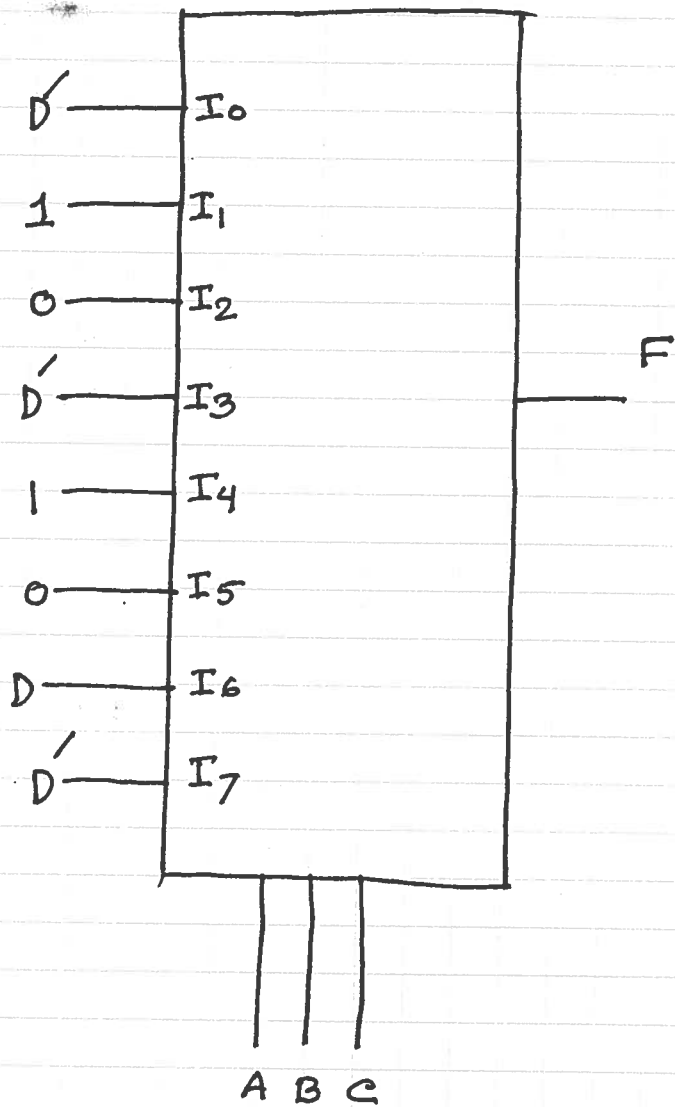


Fig: 8X1 Mux Implementation

# c) 16X1 MUX Implementation

